

Name \_\_\_\_\_

Lab Partner(s): \_\_\_\_\_

Date Performed: \_\_\_\_\_

Date Due: February 4, 2014

Physics 111 Laboratory

Experiment #3

Resistor Circuits

*Attach your fully labeled and captioned data tables for each part along with any fully labeled and captioned graphical representations of your data that you may have created to the end of this handout.*

***Honor Code Statement:***

1. Consider the simple circuit that you constructed out of one battery and one resistor. From your graphs of  $V$  vs.  $I$  for this simple circuit, what are the resistances of each resistor? How do they compare to the value given by the ohmmeter?

2. From your analysis of the simple circuit, what conclusions can you draw about the current through the resistor and the potential drop across the resistor for any given battery voltage? Is the ratio of  $\frac{V}{I}$  constant? Is Ohm's law valid for the resistor?





