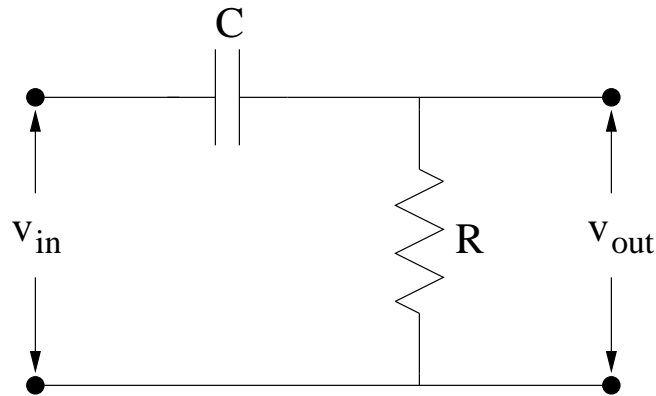


## Filter Circuits

- RC High-Pass Filter
- RC Low-Pass Filter
- Homework

## RC High-Pass Filter



$$i = \frac{v_{in}}{Z} = \frac{v_{in}}{R + \frac{1}{j\omega C}}$$

$$v_{out} = iR = \frac{R}{R + \frac{1}{j\omega C}} v_{in} = \frac{j\omega RC}{1 + j\omega RC} v_{in}$$

$$\frac{v_{out}}{v_{in}} = \frac{j\omega RC}{1 + j\omega RC}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \sqrt{\left( \frac{v_{out}}{v_{in}} \right)^* \left( \frac{v_{out}}{v_{in}} \right)} = \sqrt{\left( \frac{-j\omega RC}{1 - j\omega RC} \right) \left( \frac{j\omega RC}{1 + j\omega RC} \right)} = \sqrt{\frac{(\omega RC)^2}{1 + (\omega RC)^2}} = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

## RC High-Pass Filter (cont'd)

It is common practice to express the voltage gain (or attenuation) in decibels (dB) defined as

$$\left| \frac{v_{out}}{v_{in}} \right|_{dB} \equiv 20 \log_{10} \left| \frac{v_{out}}{v_{in}} \right|$$

$\left  \frac{v_{out}}{v_{in}} \right $	$\left  \frac{v_{out}}{v_{in}} \right _{dB}$	$\left  \frac{v_{out}}{v_{in}} \right $	$\left  \frac{v_{out}}{v_{in}} \right _{dB}$
0.01	-40	0.5	-6
0.1	-20	0.707	-3
1.0	0	1.414	+3
10.0	+20	2.0	+6
100.0	+40	4.0	+12

## RC High-Pass Filter (cont'd)



- Note that as  $\omega \rightarrow \infty$ ,  $\left| \frac{v_{out}}{v_{in}} \right| = \frac{\omega RC}{\sqrt{1+(\omega RC)^2}} \rightarrow 1.0$ , so we can write the high-frequency approximation of the gain as  $\left| \frac{v_{out}}{v_{in}} \right|_{high} \cong 1.0$
- Also note that the low frequency approximation of the gain is  $\left| \frac{v_{out}}{v_{in}} \right|_{low} \cong \omega RC \propto \omega$
- If we make a log-log graph of  $\left| \frac{v_{out}}{v_{in}} \right|$  versus  $\omega$ , we see that the actual gain can be approximated quite well by two straight lines corresponding to  $\left| \frac{v_{out}}{v_{in}} \right|_{low}$  and  $\left| \frac{v_{out}}{v_{in}} \right|_{high}$  with a sharp break or "knee" given by

$$\begin{aligned} \left| \frac{v_{out}}{v_{in}} \right|_{low} &= \left| \frac{v_{out}}{v_{in}} \right|_{high} \\ \omega_B RC &= 1 \\ \omega_B &= \frac{1}{RC} \end{aligned}$$



- At this break point, the magnitude of the gain is

$$\begin{aligned} \left| \frac{v_{out}}{v_{in}} \right| &= \frac{\omega_B RC}{\sqrt{1 + (\omega_B RC)^2}} = \frac{1}{\sqrt{2}} = 0.707 \\ \left| \frac{v_{out}}{v_{in}} \right|_{dB} &= -3 \text{ dB} \end{aligned}$$


## RC High-Pass Filter (cont'd)

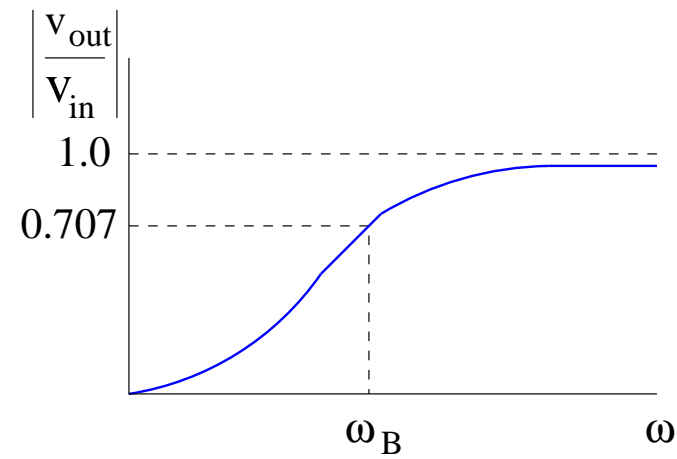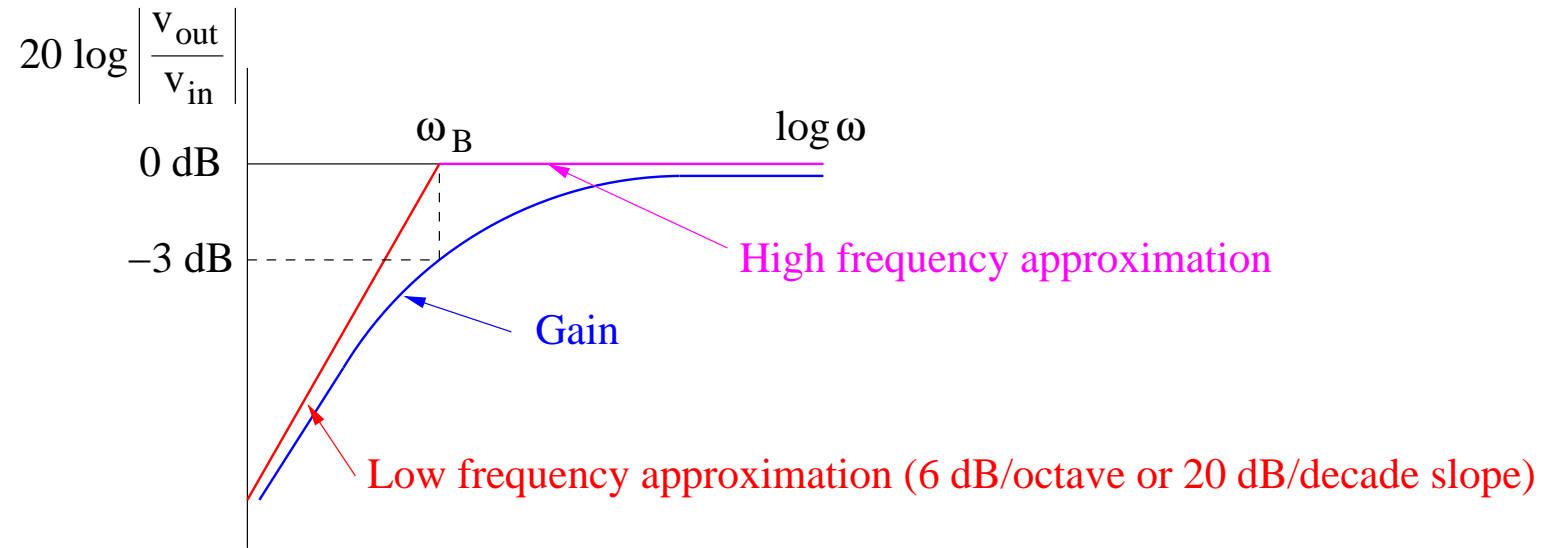

## RC High-Pass Filter (cont'd)

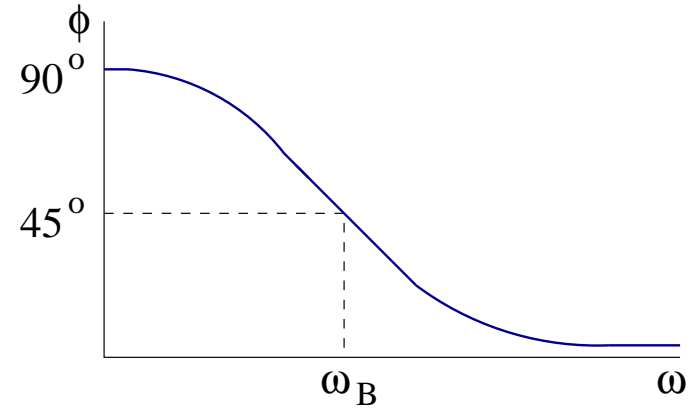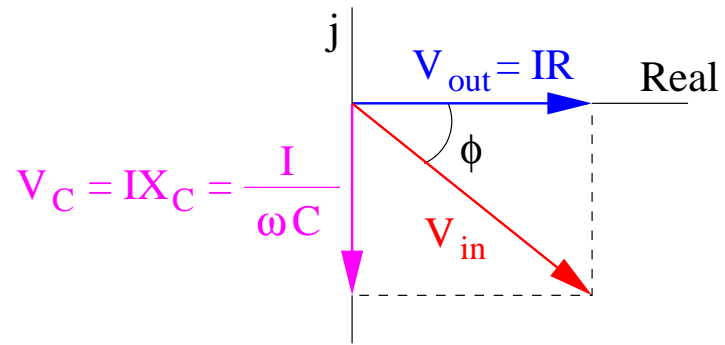

## RC Low-Pass Filter

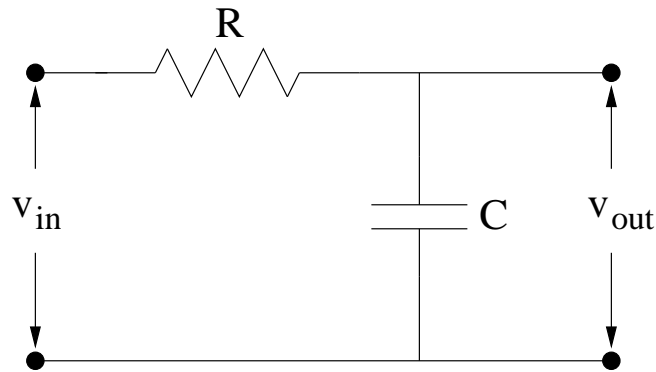

$$i = \frac{v_{in}}{Z} = \frac{v_{in}}{R + \frac{1}{j\omega C}}$$



$$v_{out} = iZ_C = \frac{i}{j\omega C} = \frac{\frac{1}{j\omega C}}{R + j\omega C} v_{in} = \frac{1}{1 + j\omega RC} v_{in}$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + j\omega RC}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \sqrt{\left( \frac{v_{out}}{v_{in}} \right)^* \left( \frac{v_{out}}{v_{in}} \right)} = \sqrt{\left( \frac{1}{1 - j\omega RC} \right) \left( \frac{1}{1 + j\omega RC} \right)} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$



Note that this goes to unity as  $\omega \rightarrow 0$ , and goes to zero as  $\omega \rightarrow \infty$

## RC Low-Pass Filter (cont'd)

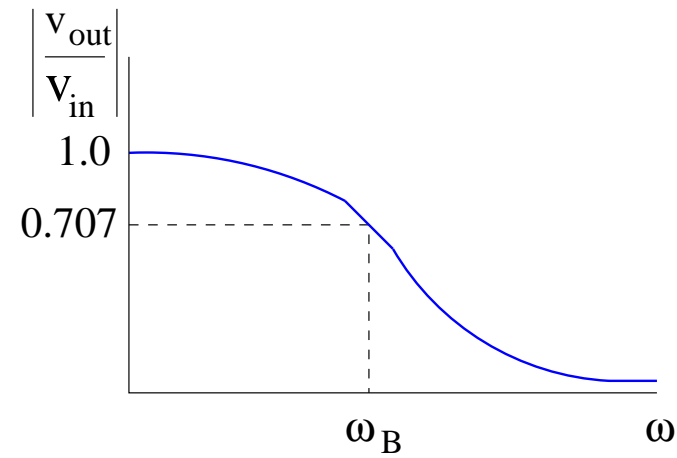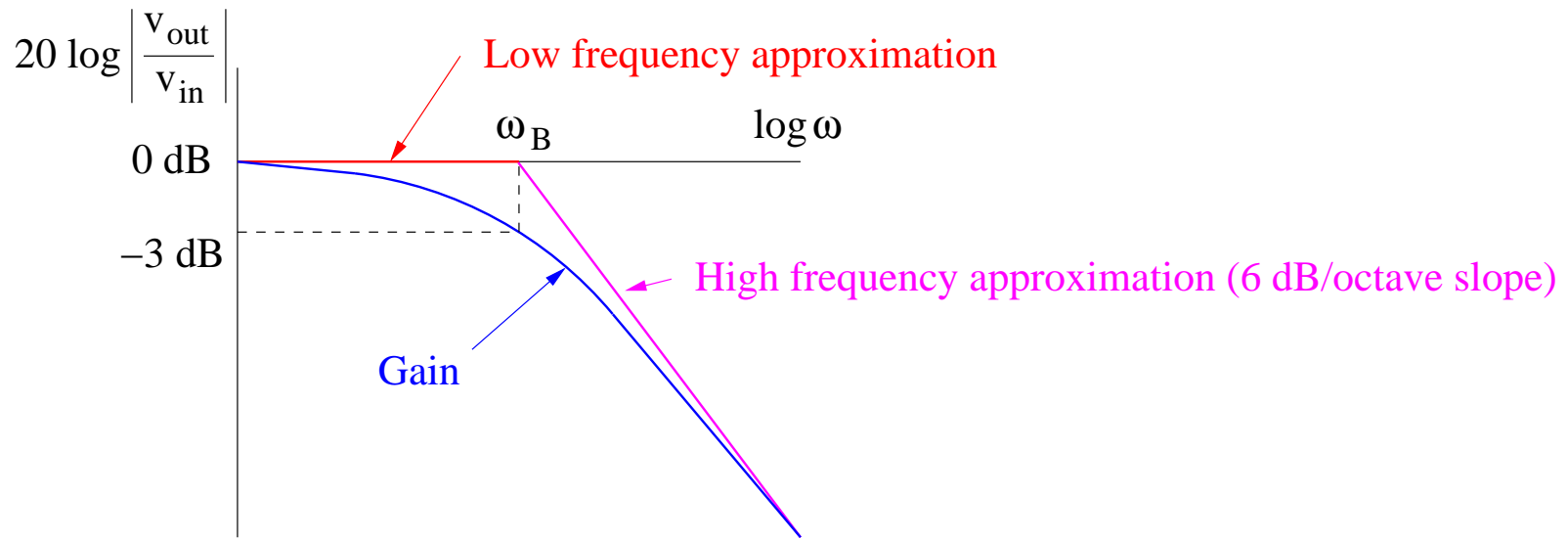



## RC Low-Pass Filter (cont'd)

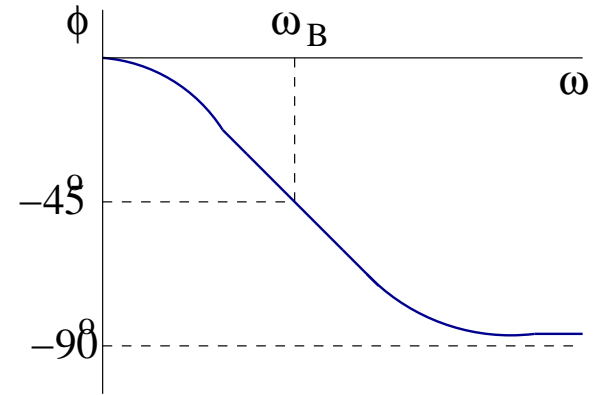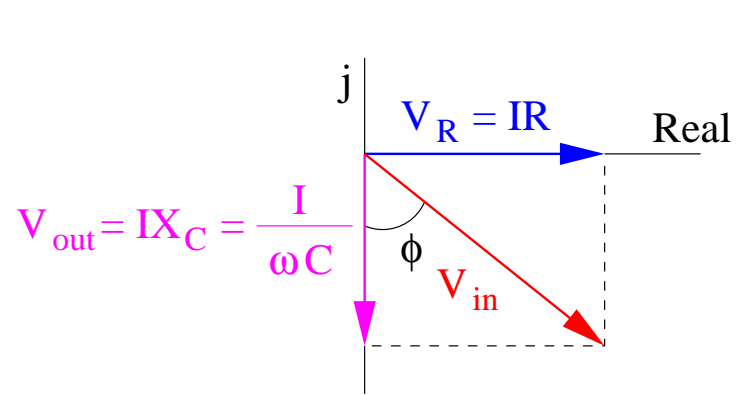

## Homework Set 18 - Due Wed. Feb. 25

1. Design a high-pass RC filter with a breakpoint at 100 kHz. Use a 1-k $\Omega$  resistor. Explain in words why the high-pass filter attenuates the low frequencies.
2. Design a low-pass RC filter that will attenuate a 60-Hz sinusoidal voltage by 12 dB relative to the dc gain. Use a 100- $\Omega$  resistor. Explain in words why the low-pass filter attenuates the high frequencies.
3. For a low-pass RC filter prove that at the frequency  $\omega = 1/RC$  the voltage gain equals 0.707.